

Remote Control Toy Car Using Arduino Uno

Abstract—This document shows how to implement remote controlled toy car using arduino.

1 COMPONENTS REQUIRED:

- 1) Arduino board
- 2) Car with Motors
- 3) L293D motor driver IC
- 4) Flysky FS-i6X 2.4GHz RC Transmitter
- 5) FS-iA10B 2.4GHz Receiver
- 6) Breadboard
- 7) Wires

2 CIRCUIT CONNECTION:

- 1) Refer the pin diagram of L293D motor driver IC

Arduino/IDE/MotorControl/Figures/pin.jpg

- 2) Connect external 9V battery to the Vcc2 pin of L293D motor driver IC
- 3) Connect Vcc1 pin to 5V output on Arduino.
- 4) The input and enable pins(ENA, IN1, IN2, IN3, IN4 and ENB) of the L293D IC are connected to six Arduino digital output pins(9, 8, 7, 5, 4 and 3).
- 5) Connect one motor to across OUT1 & OUT2 and the other motor across OUT3 & OUT4.

Arduino/IDE/MotorControl/Figures/wiring.jpg

- 6) Go to arduino IDE and Write the the following code

Arduino/IDE/MotorControl/Codes

- 7) Click on Compile and Upload the code to Arduino board.
- 8) Now you can the controll toy car using transmitter.